



## **Backup Circuit for A1080 & A1035-D**

**A description of the power supply and backup building block  
and the implication for the external circuit  
for Tyco Electronics' GPS modules  
A1080-A, A1035-D**

### **Application Note**

**Version 1.1**

**Hardware Revisions 01, 02 and 03 (A1080)**

**Hardware Revisions 01 and 02 (A1035-D)**

## Revision History

Rev.	Date	Description
1.0	07-09-07	Initial draft
1.1	08-21-08	New style; moved to Vincotech
	mm-dd-yy	

## **Disclaimer**

THIS DOCUMENT CONTAINS PROPRIETARY INFORMATION OF VINCOTECH GMBH. IT MAY NOT BE COPIED OR TRANSMITTED BY ANY MEANS, PASSED TO OTHERS, OR STORED IN ANY RETRIEVAL SYSTEM OR MEDIA, WITHOUT PRIOR CONSENT OF VINCOTECH OR ITS AUTHORIZED AGENTS.

THE INFORMATION IN THIS DOCUMENT IS, TO THE BEST OF OUR KNOWLEDGE, ENTIRELY CORRECT. HOWEVER, VINCOTECH CAN NEITHER ACCEPT LIABILITY FOR ANY INACCURACIES, OR THE CONSEQUENCES THEREOF, NOR FOR ANY LIABILITY ARISING FROM THE USE OR APPLICATION OF ANY CIRCUIT, PRODUCT, OR EXAMPLE SHOWN IN THE DOCUMENT.

THE PRODUCT (HARD- AND SOFTWARE) DESCRIBED IN THIS DOCUMENTATION IS NOT AUTHORIZED FOR USE IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF VINCOTECH.

THIS DOCUMENT MAY PROVIDE LINKS TO OTHER WORLD WIDE WEB SITES OR RESOURCES. BECAUSE VINCOTECH HAS NO CONTROL OVER SUCH SITES AND RESOURCES, VINCOTECH SHALL NOT BE RESPONSIBLE FOR THE AVAILABILITY OF SUCH EXTERNAL SITES OR RESOURCES, AND DOES NOT ENDORSE AND IS NOT RESPONSIBLE OR LIABLE FOR ANY CONTENT, ADVERTISING, PRODUCTS, OR OTHER MATERIALS ON OR AVAILABLE FROM SUCH SITES OR RESOURCES. VINCOTECH SHALL NOT BE RESPONSIBLE OR LIABLE, DIRECTLY OR INDIRECTLY, FOR ANY DAMAGE OR LOSS CAUSED OR ALLEGED TO BE CAUSED BY OR IN CONNECTION WITH USE OF OR RELIANCE ON ANY SUCH CONTENT, GOODS OR SERVICES AVAILABLE ON OR THROUGH ANY SUCH SITE OR RESOURCE.

VINCOTECH RESERVES THE RIGHT TO CHANGE, MODIFY, OR IMPROVE THIS DOCUMENT OR THE PRODUCT DESCRIBED HEREIN, AS SEEN FIT BY VINCOTECH WITHOUT FURTHER NOTICE.

## Table of Contents

<b>1 Introduction .....</b>	<b>5</b>
<b>2 Backup and Main Power Supply .....</b>	<b>5</b>
2.1 Power Supply Building Block of the A1080 and A1035-D .....	5
2.2 Application Examples .....	6
2.2.1 Application without Backup Support .....	6
2.2.2 Application using a Electrochemical Double Layer Capacitor .....	6
2.2.3 Application using a Primary Cell .....	6
2.2.4 Application using a Fixed Voltage Source .....	7
2.2.5 Application using a Rechargeable Battery .....	7
<b>3 Related Information .....</b>	<b>8</b>
3.1 Contact .....	8
3.2 Related Documents .....	8

## 1 Introduction

This document briefly describes the power supply and backup block built into the GPS receivers A1080 and A1035-D and the implications for the external circuitry.

## 2 Backup and Main Power Supply

### 2.1 Power Supply Building Block of the A1080 and A1035-D

Fig. 1 shows the simplified power supply circuit of the A1080 and A1035-D. Basically two different supply domains are present. The main voltage regulator (IC1, 2.8V) is responsible for all the loads present at full operation (e.g. CPUs, RF oscillator, down-converter), the backup voltage regulator (IC2, 1.5V) supplies current to all parts of the circuit that should continue to work if only  $V_{BAK}$  is supplied (mainly battery backed SRAM and real time clock).

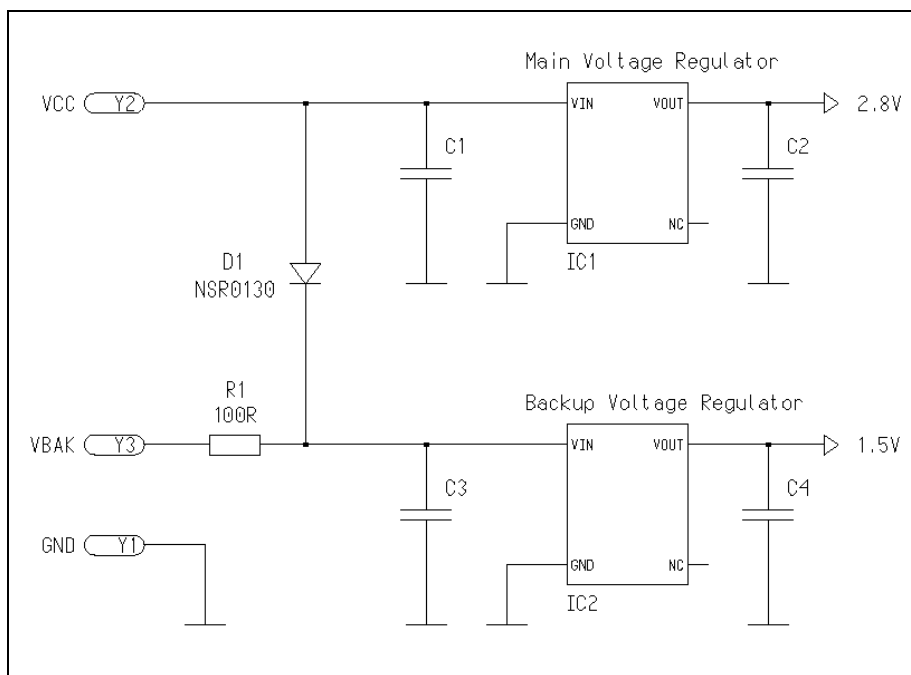


Fig. 1: Voltage Regulators on GPS Receiver A1080 and A1035-D

For further understanding it is important to notice that both regulators need to be active during fully operational mode of the GPS module.


## 2.2 Application Examples

This section presents some common applications examples of how to use the  $V_{BAK}$  pin of the A1080 and A1035-D GPS receiver module. It covers situation with no backup at all and solutions with fixed voltages and several rechargeable devices. Each example provides a schematic of the circuit that is typically connected to the  $V_{BAK}$  pin for that specific application.

### 2.2.1 Application without Backup Support


In application that do not demand SRAM and RTC backup at all it is safe to power the A1080 only through the  $V_{CC}$  pin. The diode D1 provides power also to the backup domain. In that case it is suggested to leave the  $V_{BAK}$  pin open.
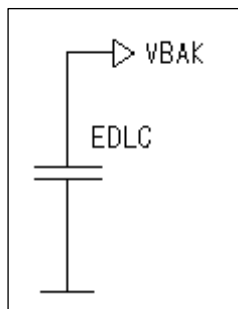
### 2.2.2 Application using a Electrochemical Double Layer Capacitor



One common device to store backup power is an electrochemical double layer capacitor (EDLC, often referred to as Gold- or Supercap). Before this device is able to supply power it needs to be charged. An EDLC connected between GND and  $V_{BAK}$  is charged through D1 and R1 up to supply voltage applied to the  $V_{CC}$  pin. As with any capacitor there is no risk of destroying the device due to excessive charging, thus no special care has to be taken. Charge current will automatically drop to zero as soon as the voltage over the capacitor has reached the supply voltage. If the main power supply is removed the backup domain is still supplied by the EDLC through the  $V_{BAK}$  pin. Now D1 prevents current from flowing towards the main power regulator. As long as the voltage is above the minimum voltage necessary for SRAM and RTC retention the data remains valid. Please see the separate application note for more details about EDLCs.
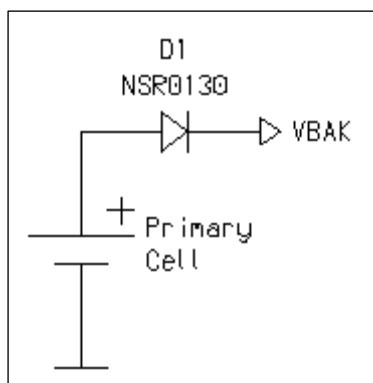
### 2.2.3 Application using a Primary Cell




In order to avoid severe problems with leaking or even exploding primary cells (e.g. lithium button cells) any current into the battery should be avoided under all circumstances. As the A1080 and A1035-D were deliberately designed to charge a capacitor attached to the  $V_{BAK}$  pin an external diode D1 connected in series is strongly recommended.

However, there is one very important detail to consider. Due to the fact that the backup domain is fed by two sources (main power and external battery) decoupled through diodes the actual current (approximately  $20\mu A$ ) is delivered by the source

with the higher voltage. Thus, to avoid unnecessary draining of the backup battery, it is strongly recommended to set the main voltage  $V_{CC}$  slightly higher than the battery voltage  $V_{BAK}$ . Please check the receiver manuals for absolute maximum ratings.

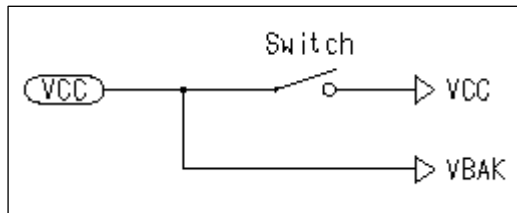
### 2.2.4 Application using a Fixed Voltage Source



The primary cell (see section 2.2.3) can be replaced by a fixed voltage source, e.g. some standby supply available in the system anyway. In case the voltage level is different from the main power supply the same restriction as mentioned in section 2.2.3 apply. In

case the voltage level is identical the diode can be omitted. Replacing the mechanical switch in the schematic by a transistor (e.g. a p-channel power MOSFET) will provide functionality similar to the ENABLE pin present on the A1029 GPS receiver.
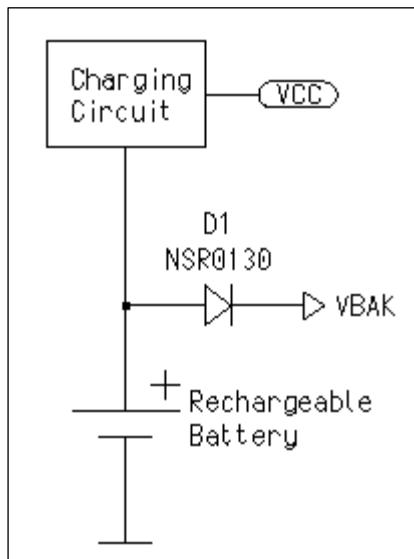
### 2.2.5 Application using a Rechargeable Battery



The A1080 and A1035-D GPS receivers are designed to charge an EDLC attached to the  $V_{BAK}$  pin. However, this is not an appropriate solution for a rechargeable battery since to provision against excessive charging is implemented. Thus it is strongly recommended to use an external charging circuit suitable for the specific chemistry of the battery. Again, the decoupling diode D1 is essential and the comments regarding voltage levels and resulting currents as described in section 2.2.3 apply.

## **3 Related Information**

### **3.1 Contact**

This manual was created with due diligence. We hope that it will be helpful to the user to get the most out of the GPS module.

Anyway, inputs about errors or mistakable verbalizations and comments or proposals to Vincotech, Germany, for further improvements are highly appreciated.

#### **Vincotech GmbH**

Bibergerstr. 93  
82008 Unterhaching (Munich)  
Germany

Tel.: +49 89 8780 67 0

Fax: +49 89 8780 67 351

[gps@vincotech.com](mailto:gps@vincotech.com)

[www.vincotech.com/gps](http://www.vincotech.com/gps)

### **3.2 Related Documents**

- GPS Receiver A1080 (Vincotech)
- GPS Receiver A1035-D (Vincotech)
- AppNote GPS EDLC Backup A1080 & A1035-D (Vincotech)
- GPS Receiver A1029 (Vincotech)